

MOS Characteristics II


zrrraa

2023.11.14

I/V Characteristics

Case I: $V_{DS} < V_{GS} - V_{TH}$

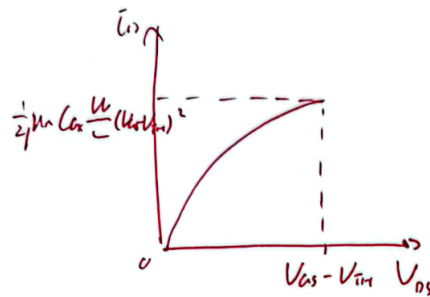Last day we know the $I_D - V_{DS}$ relationship when $V_{DS} \leq V_{GS} - V_{TH}$.



The $I_D - V_{DS}$ relationship when $V_{DS} \leq V_{GS} - V_{TH}$


The drain current is:

$$I_D = \mu_n * C_{ox} * \frac{W}{L} [(V_{GS} - V_{TH}) * V_{DS} - \frac{1}{2} V_{DS}^2]$$

We now assume that $V_{DS} * (V_{GS} - V_{TH}) \gg \frac{1}{2} V_{DS}^2$, that is $V_{DS} \ll 2(V_{GS} - V_{TH})$.
we can get:

$$I_D \approx \mu * C_{ox} \frac{W}{L} * (V_{GS} - V_{TH}) * V_{DS}$$

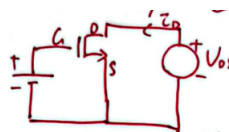
That is, V_{DS} is linearly related to I_D , shows us that **A MOSFET can act as a voltage-dependence resistor.** (if $V_{DS} \ll 2(V_{GS} - V_{TH})$)



$$R_{on} = \frac{V_{DS}}{I_D} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$

R_{on} means the resistance when the MOS turns on.


MOS Device as a Switch

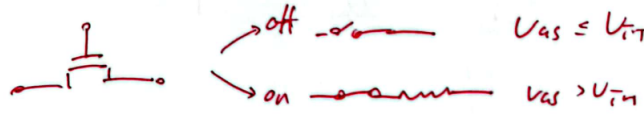

MOS device as a switch

For example, it can use in a Bluetooth System, for both side have to determine to transmit or receive.

Case II: $V_{DS} > V_{GS} - V_{TH}$

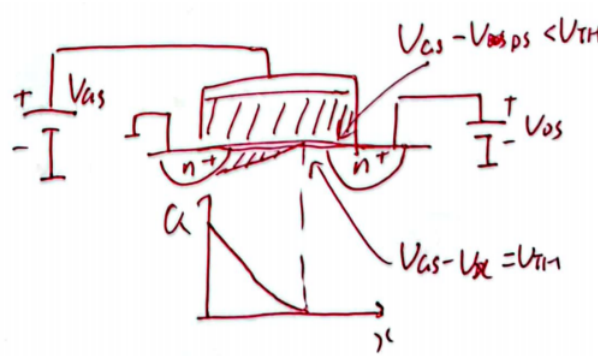

Pinch-off

The potential difference between the upper and lower plates at the drain end is less than V_{TH} , leads to no electronics exit.

We call this phenomenon **pinch-off**.

Rederive I/V Equation

Relationship between I_D and V_{DS}

$$\int_0^L I_D dx = \mu_n * W * C_{ox} * \int_0^{V_{GS} - V_{TH}} (V_{GS} - V_{TH} - V(x)) dV$$


Compare to the equation we derive last day, there we assume that the point of pinch-off close to the Drain. So the upper limit of the integral on the left-hand side of the equation is still L.

The upper limit of the integral on the right-hand side of the equation changes. For only $V_{GS} - V(x) > V_{TH}$ there exists Q.

$$I_D L = \frac{1}{2} \mu C_{ox} W (V_{GS} - V_{TH})^2$$


$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

Then we can draw the complete curve.

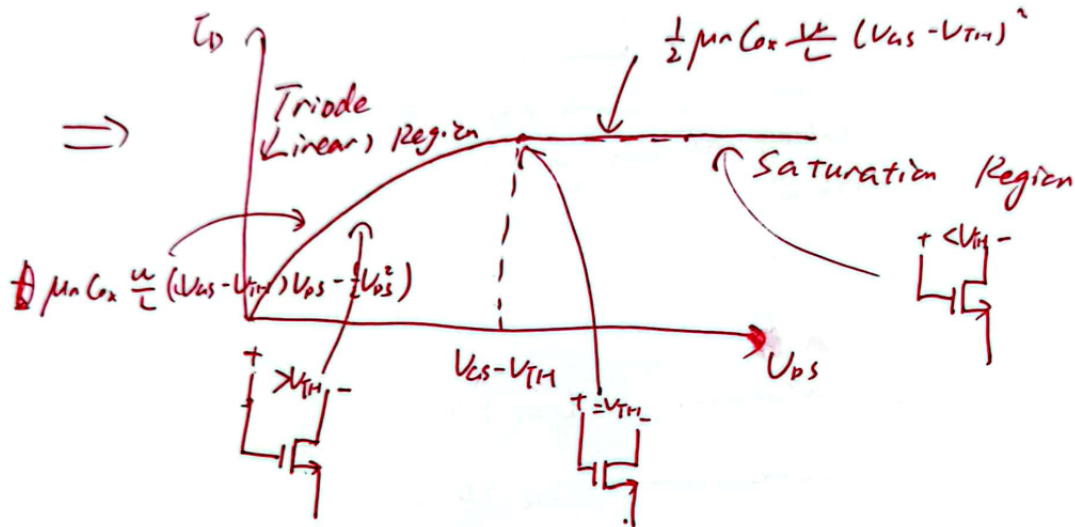

Relationship between I_D and V_{DS}

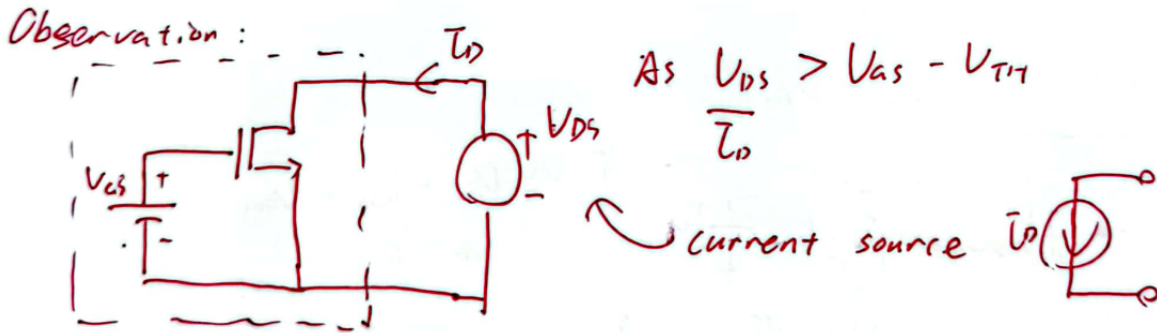This also enlightens us that we only need to pay attention to the potential difference between the G and the D to judge the saturation region and the linear region. as the picture shows.




Current Source

As $V_{DS} > V_{GS} - V_{TH}$, the I_D is a constant. We can use this to make a current source.

Relationship between I_D and V_{GS}

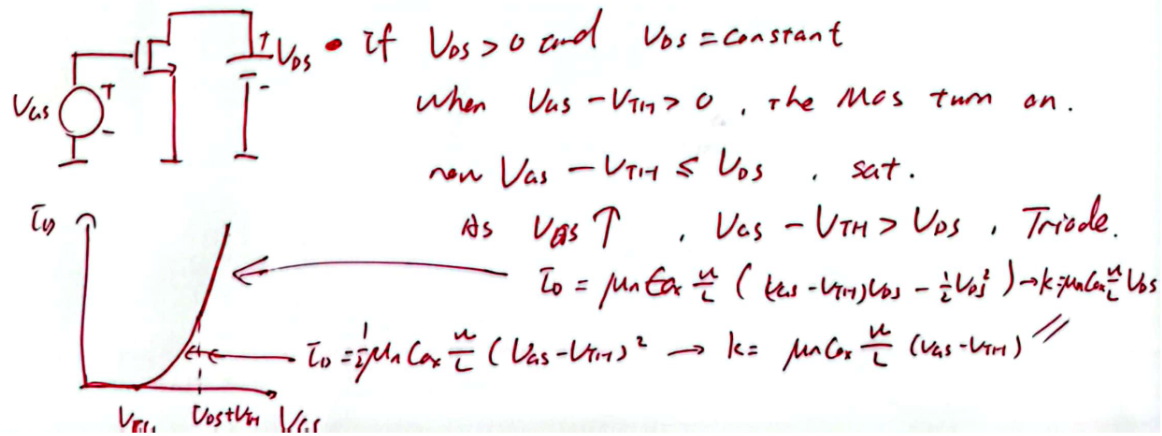We can also derive the relationship between I_D and V_{GS} .




Relationship between I_D and V_{GS}

If $V_{DS} > 0$ and V_{DS} is a constant, when $V_{GS} > V_{TH} > 0$, the MOS turns on. now $V_{GS} - V_{TH} \leq V_{DS}$, the MOS is in saturation zone.

As V_{GS} becomes larger, $V_{GS} - V_{TH} > V_{DS}$, the MOS is in triode zone.

We can calculate for the curve, as I show in the picture.

Simple Model in Saturation Zone

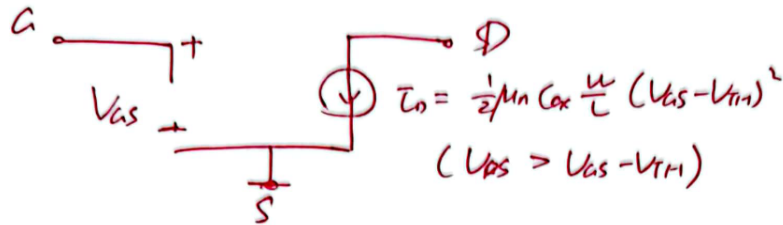

Use the Saturation to Design a Current Source

Example

$$\mu C_{ox} = 100 \mu A/V^2, V_{TH} = 0.5V, \frac{W}{L} = \frac{5 \mu m}{0.5 \mu m}$$

Design a 1mA current source.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

we get $V_{GS} = 1.91V$.

Therefore, when $V_{DS} \geq 1.41V$, the MOS can be a current source with $I_D = 1mA$.

Link

Razavi Electronics Circuits 1: lectrue 31