 


MOS Small-Signal Model, PMOS Device

zrrraa

2023.11.17


Large-Signal & Small-Signal Operation



Large-Signal & Small-Signal Operation


Small-Signal Models of Const Sources

 In const sources, we make all constants equal 0.



Small-Signal Models of Const Sources

Here's a example.

 

General Procedure of Constructing a Small-Signal Model

- Apply proper bias voltages to the device.
- Increment the voltage difference between two terminals.
- Measure all current increments.
- Model the change by a proper electrical device.



Increment of V_{GS}

In the second point above, we want to study the effect of the voltage increment at the two terminals on the circuit. Let's take a look at the impact of increasing V_{DS} on the circuit.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

Now we take consideration of the Channel-Length Modulation, so the increment of V_{DS} leads to the increment of I_D .

$$I_D + \Delta I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS} + \lambda \Delta V_{DS})$$

$$I_D + \Delta I_D = I_D + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda \Delta V_{DS}$$


Here we regard $\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$ approximately as I_D .

So we can get:


$$\frac{\Delta V_{DS}}{\Delta I_D} \approx \frac{1}{\lambda I_D} = r_o$$

We think of the connection between drain and source as a resistor.

 Neglect the effect of Channel-Length Modulation on the g_m expressions. Here's the small-signal model with r_o .




 Think of the connection between drain and source as a resistor



Small-Signal model with r_o

Example

 

$$V_{GS} - V_{TH} \leq V_{DS} \implies \text{Saturation}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \implies r_o = \frac{1}{\lambda I_D} \implies r_o = 20.4 k\Omega$$


$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \frac{1}{1.43 k\Omega}$$

PMOS

For PMOS:


- $V_G < V_S$
- $V_{TH} < 0$
- $V_D < V_S$

 In PMOS, the Gate voltage is minus, so it can attract the holes to form the channel. The current flows from Source to Drain.




Large-Signal Model

 Pay attention, I_D is still defined from Drain to Source. So it's minus.



Small-Signal Model

 

Link

[Razavi Electronics Circuits 1: lectrue 34](#)