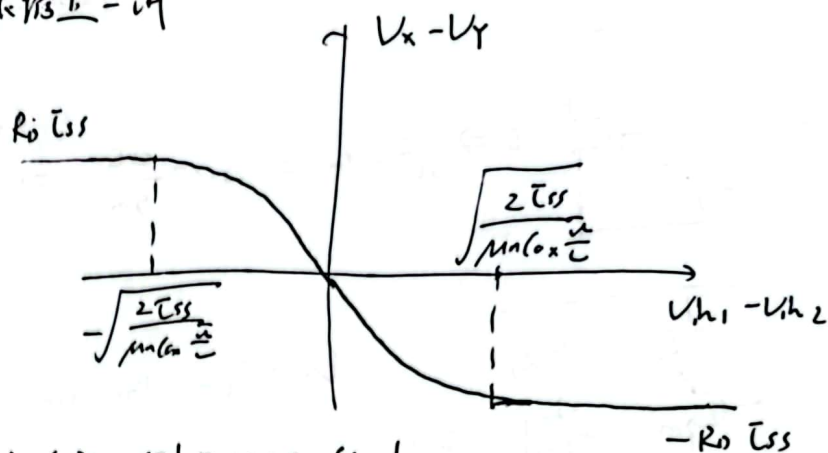


for  $\beta_3 \downarrow - \downarrow$



$V_{h1} - V_{h2} \gg \sqrt{2Iss / (\mu Cox \frac{W}{L})}$ ,  $V_{h1} \approx V_{h2} \approx V_{TH}$  MOS off of

if  $V_{h1} - V_{h2} \gg \sqrt{2Iss / (\mu Cox \frac{W}{L})}$ ,  $M_2$  off

$$V_{h2} - V_{TH} = V_0$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{h1} - V_{TH})^2 = I_{SS} \Rightarrow V_{h1} - V_0 - V_{TH} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$V_{h1} - V_{h2} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$\text{又有 } I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{h1} - V_{h2}) \sqrt{\frac{4 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{h1} - V_{h2})^2}$$

$$\Rightarrow V_x - V_y = -\frac{R_D}{2} \mu_n C_{ox} \frac{W}{L} (V_{h1} - V_{h2}) \sqrt{\frac{4 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{h1} - V_{h2})^2}$$

If  $(V_{h1} - V_{h2})^2 \ll \frac{4 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}$ , at origin point

$$V_x - V_y = -\frac{R_D}{2} \mu_n C_{ox} \frac{W}{L} \sqrt{\frac{4 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} (V_{h1} - V_{h2})$$

$$= -R_D \mu_n C_{ox} \frac{W}{L} \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} (V_{h1} - V_{h2})$$

$$= -R_D \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (V_{h1} - V_{h2})$$


when close to origin point,  $k = -R_D \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$

①  $I_{SS}$  is doubled. slope changes to  $k = -\sqrt{\mu_n C_{ox} \frac{W}{L} 2 I_{SS}} R_D$

the circuit becomes more linear because it can take a larger input difference without "dying".


②  $\frac{W}{L}$  is doubled.

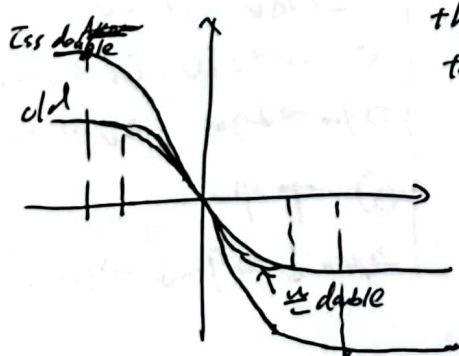The circuit becomes less linear, because it can take only a smaller input difference before it "dies".




# Small-Signal Behavior of MOS Diff Pair.

A few points.

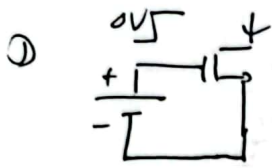
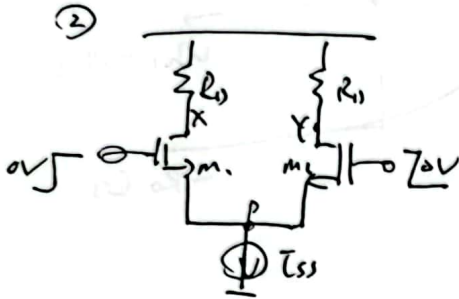
$$\Delta I \Rightarrow \frac{\Delta I}{\Delta V} = g_m \Rightarrow \Delta V = \frac{\Delta I}{g_m} \Rightarrow$$



$$V_x - V_y = -R_D \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} \cdot (2\Delta V)$$

$$\Rightarrow \therefore V_x - V_y = -R_D (I_{D1} - I_{D2})$$

$$\Rightarrow \begin{cases} I_{D1} - I_{D2} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (2\Delta V) \\ I_{D1} + I_{D2} = I_{SS} \end{cases}$$


$$\Rightarrow I_{D1} = \frac{I_{SS}}{2} + \underbrace{\sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} \Delta V}_{\Delta I}$$

$$\therefore \frac{\sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} \Delta V}{\Delta I} = g_m = \Delta V \Rightarrow g_m = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$$


与偏置电压有关

$V_p$  doesn't change  $\Rightarrow$  P is AEGND.  
CS stage

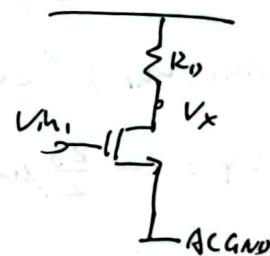
$$\Rightarrow \frac{V_x}{V_{in1}} = -g_m R_D \Rightarrow \frac{V_x - V_p}{V_{in1} - V_{in2}} = -g_m R_D$$



Example

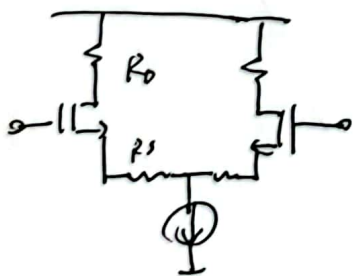
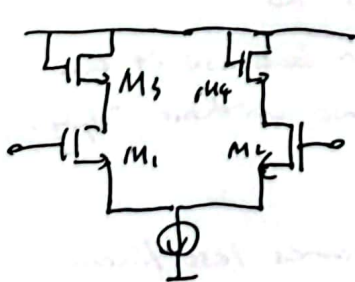
$$\frac{V_x}{V_{in1}} = -\frac{R_D}{\frac{1}{g_m} + R_S} \quad \text{degeneration.}$$



$$\frac{V_x}{V_{in1}} = -\frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S} = -g_{m1} \frac{1}{g_{m2} + \frac{1}{R_S}}$$

Observations

①  $W \rightarrow 2W$ .

$$\Rightarrow g_m \rightarrow \sqrt{2} g_m$$

$$\Rightarrow A_v \rightarrow \sqrt{2} A_v$$


②  $W \rightarrow 2W, I_{SS} \rightarrow 2I_{SS}$

$$\Rightarrow g_m \rightarrow 2g_m, A_v \rightarrow 2A_v$$


③  $T \uparrow$

$$\Rightarrow \mu_n \downarrow \Rightarrow g_m \downarrow \Rightarrow |A_v| \downarrow$$

## P-Type Diff Pair

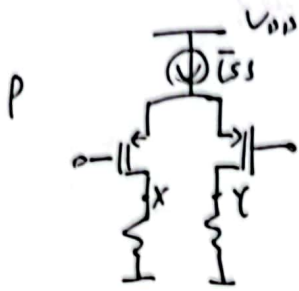


the same as N-Type


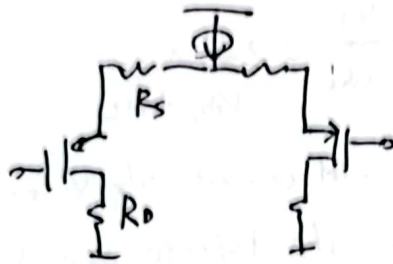


$$A_v = - \frac{R_D}{\frac{1}{g_m} + R_S}$$

## Example

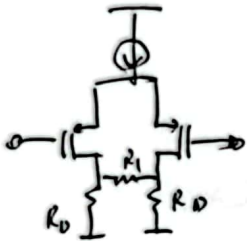


同相. 差分

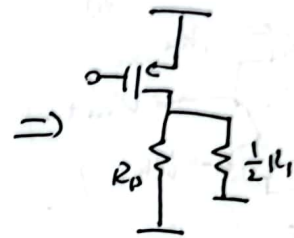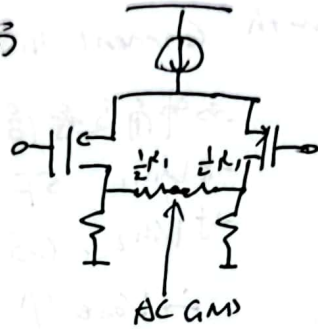

$$\therefore \frac{V_X}{V_{in}} = -g_m(R_D \parallel \frac{1}{2}R_1)$$

## Diff. Pair with Current-Source Loads.

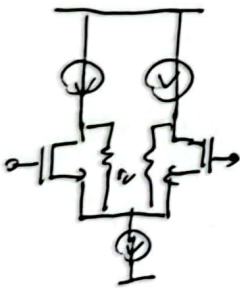


$A_v = -g_m R_{D1}$ . if we want a large  $A_v$ , we need a large  $R_{D1}$ . That's why we use current-source.

In this case, the  $r_o$  can't be ignored.


$$A_v = -g_m r_o.$$

## Diff. Pair with Cascodes.

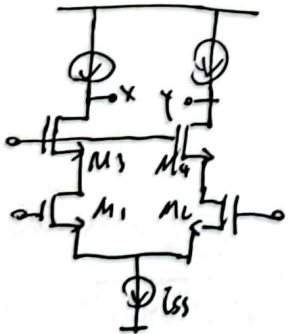

$$A_v = -g_{m1} \left[ (1 + g_{m3} r_{o3}) r_{o1} + r_{o3} \right] \approx -g_{m1} g_{m3} r_{o3} r_{o1}$$

Let's implement the current sources.

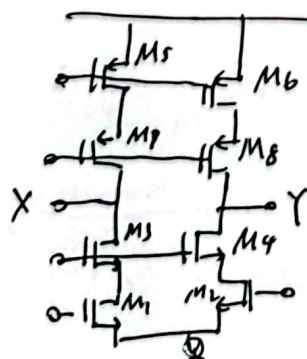


"Telescopic Cascode"

$$A_v = -g_{m1} \left[ (1 + g_{m3} r_{o3} r_{o1} + r_{o3}) \parallel (1 + g_{m7} r_{o7} + r_{o7}) \right]$$



Diff. Pair with Active Load.

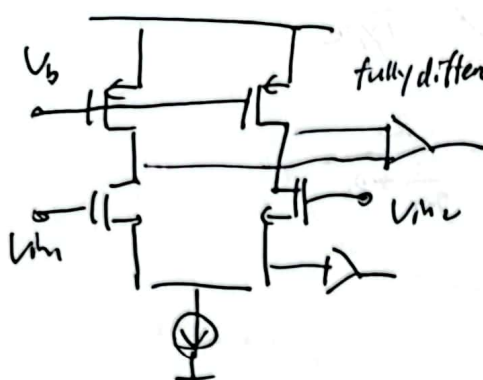

→ 放大


$$\frac{V_x - V_y}{V_{in1} - V_{in2}} = 2 \frac{V_x}{V_{in1} - V_{in2}}$$

We could connect only X to A and simply not use Y. the voltage gain is halved.

single-ended.



Single-ended

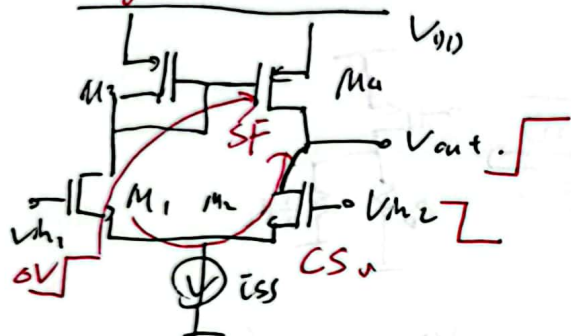

with Current Mirror.


→ 中角反看信号变化趋势.

对 \$V\_{in1}\$, SF, \$V\_{out}\$ 同向变化

对 \$V\_{in2}\$, CS, \$V\_{out}\$ 反向变化.

→ \$V\_{out} \uparrow\$. 是 \$V\_{in2}\$ 反相放大.

Draw Small-Signal Model

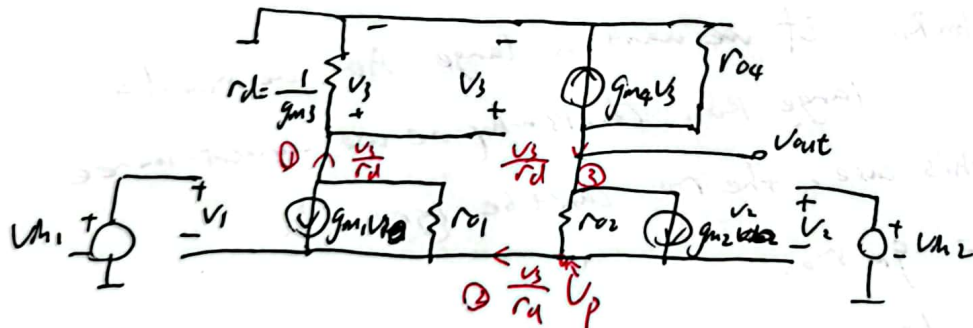

3个节点... KCL

$$① \frac{V_s}{r_{d1}} + g_{m1} V_1 + \frac{V_s V_1}{r_{o1}} = 0$$

$$② -\frac{V_s}{r_{d1}} + g_{m2} V_2 + \frac{V_{out} - V_s}{r_{o2}} = 0$$

$$③ g_{m4} V_s + \frac{V_{out}}{r_{o4}} + \frac{V_s}{r_{d1}} = 0 \Rightarrow V_s = \frac{-V_{out}}{r_{o4}(\frac{1}{r_{d1}} + g_{m4})} = -\frac{V_{out}}{r_{o4} \times 2g_{mp}}$$


$$\therefore V_{in1} - V_{in2} = V_1 - V_2$$

$$\therefore \text{由 } ① \text{ 和 } ② \text{ 得: } g_{mN}(V_{in1} - V_{in2}) + \frac{V_s - V_{out}}{r_{on}} + \frac{2V_s}{r_{d1}} = 0$$

$$\Rightarrow \frac{V_{out}}{V_{in1} - V_{in2}} = g_{mN}(r_{on} || r_{op}) \leftarrow g_{mN}(V_{in1} - V_{in2}) = V_{out} \left( \frac{1}{2g_{mp}r_{op}r_{on}} + \frac{1}{r_{on}} + \frac{1}{r_{d1}} \right)$$


在 fully differential 中.

$$\frac{V_x - V_y}{V_{in1} - V_{in2}} = -g_{mN} (r_{on} || r_{op})$$

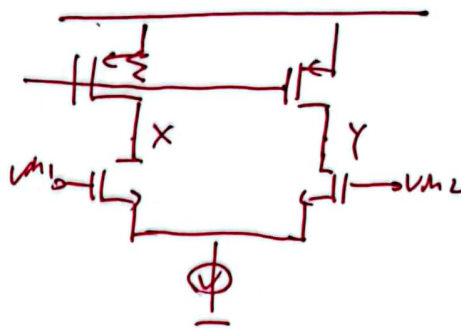

单端放大达到了同样的增益.

以下是一些 common 的电路

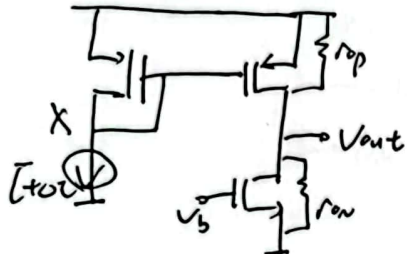


$$\Delta V_x = \Delta I \cdot \left( \frac{1}{g_m} || r_o \right) \approx \frac{\Delta I}{g_{mp}}$$

$$\frac{\Delta V_{out}}{\Delta V_x} = -g_{mp} (r_{on} || r_{op})$$

$$\Rightarrow \Delta V_{out} = -\Delta I (r_{on} || r_{op})$$

据此公式也可在 ~~该~~ ~~电路~~ 单端放大公式.

$$\Delta V_{out} = -\Delta I (r_{on} || r_{op})$$

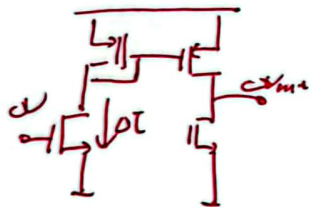

$$\Delta I = \Delta V \cdot g_{mN}$$

$$\therefore \frac{\Delta V_{out}}{\Delta V} = -g_{mN} (r_{on} || r_{op})$$