

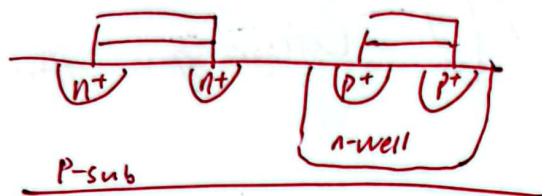


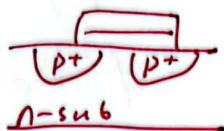

CMOS Technology


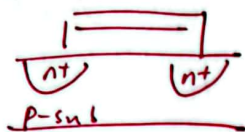


expensive, but worth it.

Example


$$V_{THN} = 0.5V$$

$$V_{THP} = -0.6V$$

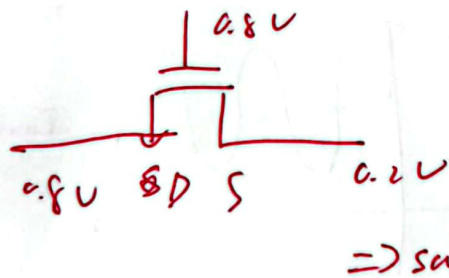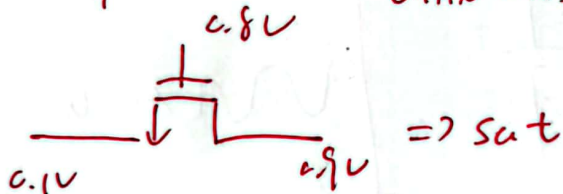


the arrow only indicates the N/P mos
but not the D or S.

so here the left is D, right is S

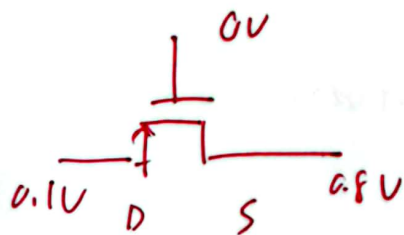

$$(0.1V - 0V) < |0.6V| \Rightarrow \text{sat.}$$

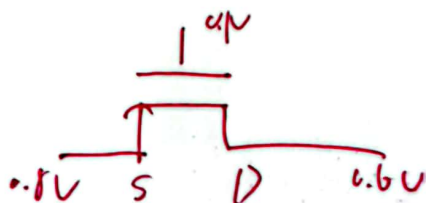


$$0.5V < |-0.6V| \Rightarrow \text{sat.}$$

CMOS Amplifiers




• Amp design procedure

- ① select an amp topology
- ② Bias the transistor(s) to obtain proper values for g_m, r_o, \dots
- ③ Determine the characteristics of the circuit.

• Amp Characteristics

- ① Gain  Voltage gain A_v .
- ② Power Dissipation
- ③ ...

Let's build an amp

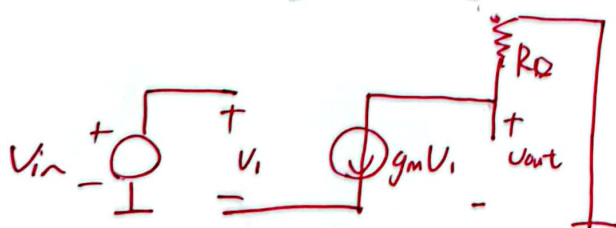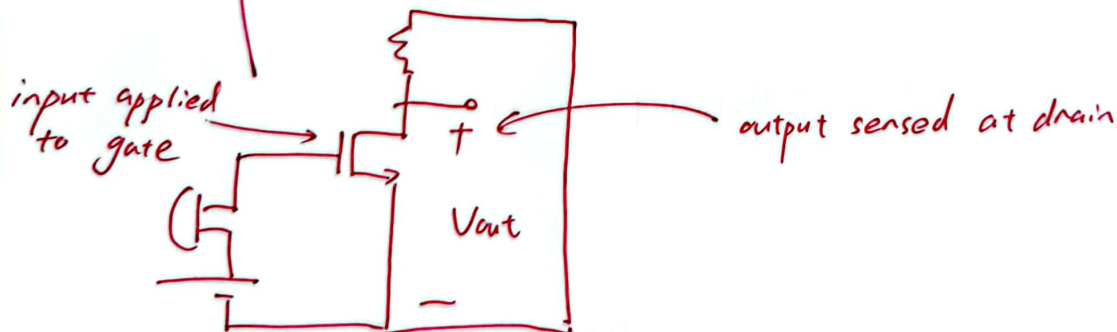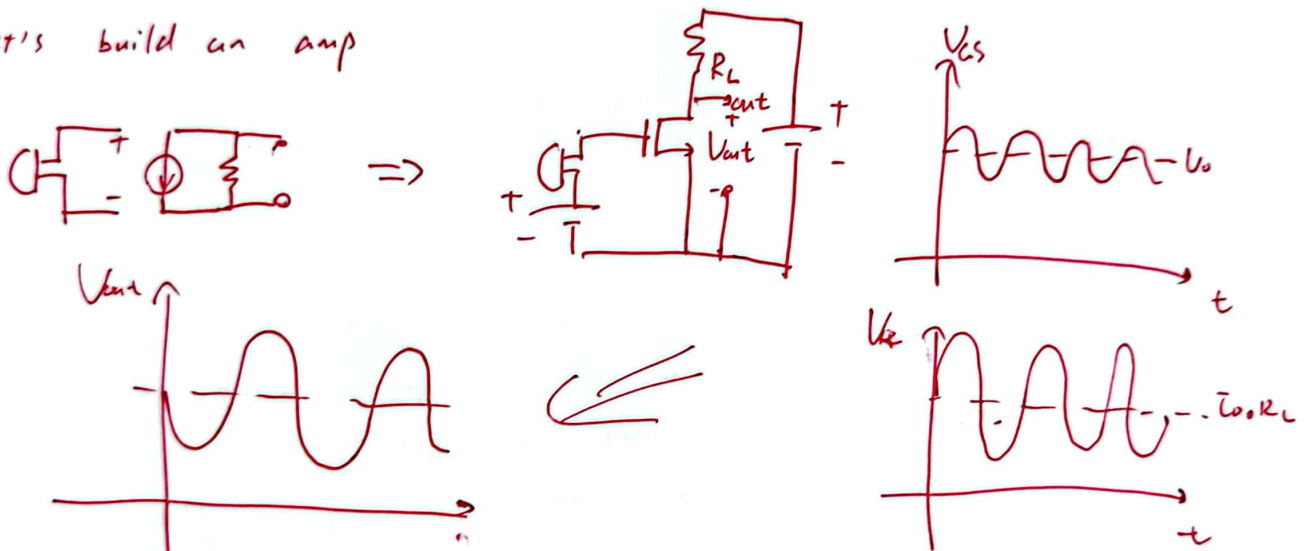

$$\frac{V_{out}}{R_D} + g_m V_i = 0 \Rightarrow \frac{V_{out}}{V_{in}} = -g_m R_D$$