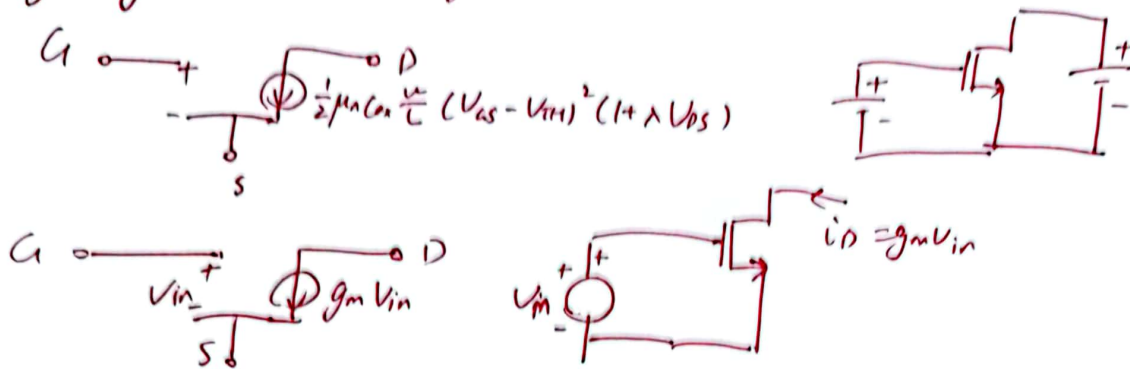



Large-Signal & Small-Signal Models (in Sat)



Small-Signal Models of Constant Sources


$$\frac{I}{V} \Rightarrow \text{short} \quad V \rightarrow 0$$
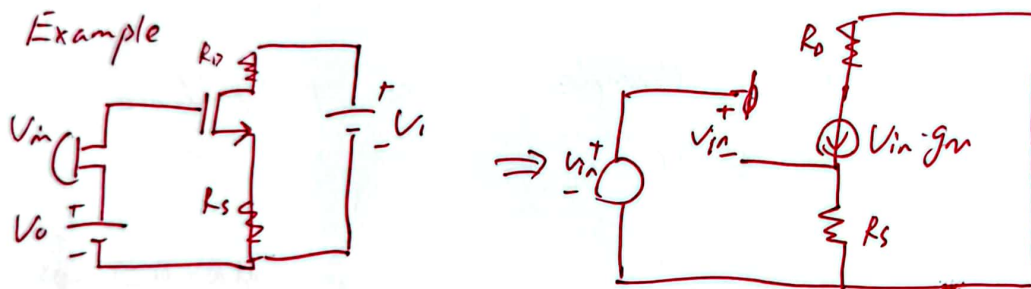
$$\frac{V}{I} \Rightarrow \text{open} \quad I \rightarrow 0$$



General Procedure of Constructing a Small-Signal Model

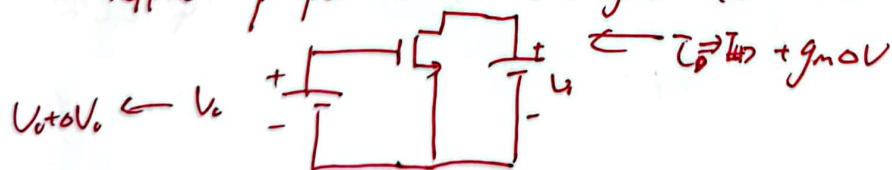
- ① Apply proper bias voltages to the device



- ② Increment the voltage difference between two terminals
- ③ Measure all current increments
- ④ Model the change by a proper electrical device.



Increment of V_{DS}

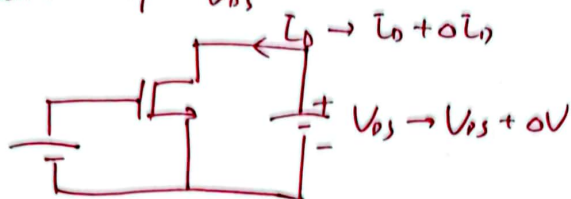

because of +ve ^{length} channel-Modulation



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$I_D + \Delta I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS} + \lambda \Delta V_{DS})$$


$$I_D + \Delta I_D = I_D + \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2}_{\approx I_D} \lambda \Delta V_{DS}$$

$$\frac{\Delta V_{DS}}{\Delta I_D} \approx \frac{1}{\lambda I_D} = r_o$$

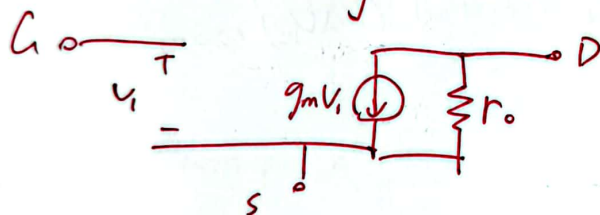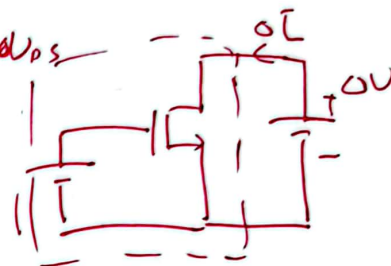We neglect the effect of channel-length modulation on the g_m expressions



Example

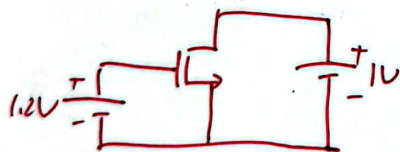

$$\mu_n C_{ox} = 100 \mu A/V^2 \quad \frac{W}{L} = 10$$

$$V_{TH} = 0.5V$$



$$\lambda = 0.2 V^{-1}$$

$$V_{GS} - V_{TH} \leq V_{DS} \Rightarrow \text{sat.}$$





$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \Rightarrow r_o = \frac{1}{\lambda I_D} \Rightarrow r_o = 20.4 k\Omega$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \frac{1}{1.43 k\Omega}$$

MOS device Types

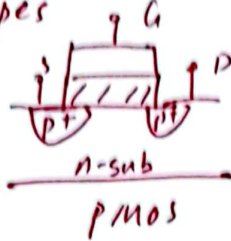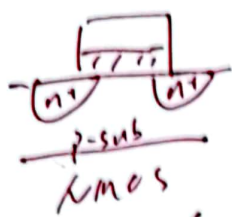

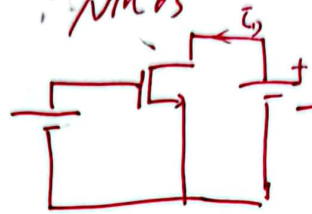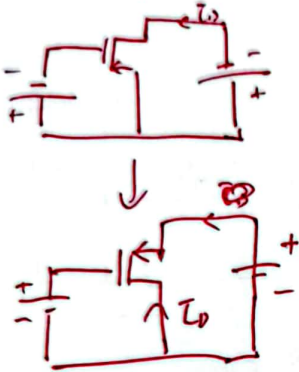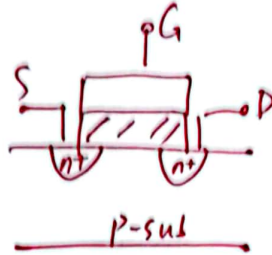
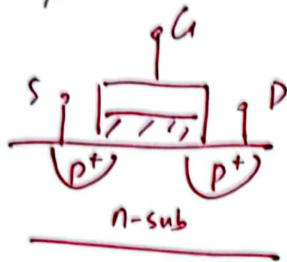
$$\begin{aligned} V_G &< V_S \\ V_{TH} &< 0 \\ V_D &< V_S \end{aligned}$$




In Sat.

$$I_D = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 - \lambda V_{DS}) \quad (\lambda > 0)$$

Large-Signal Model

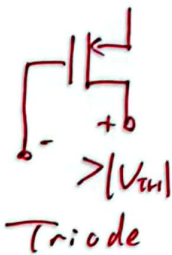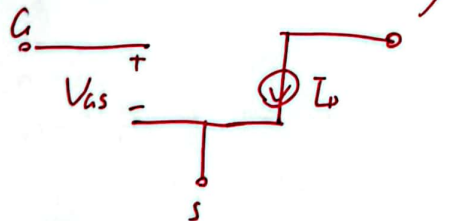

Triode

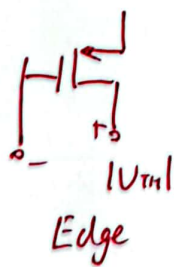

Edge



Sat.

Small-Signal Model

