
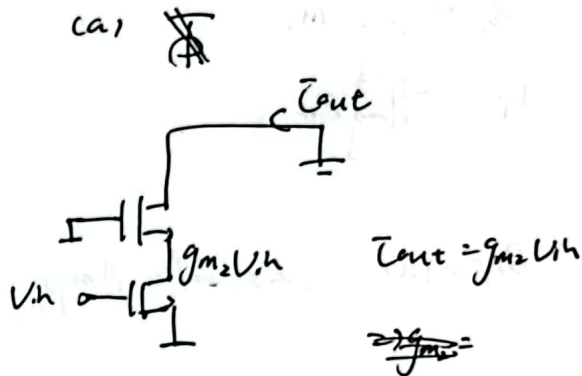


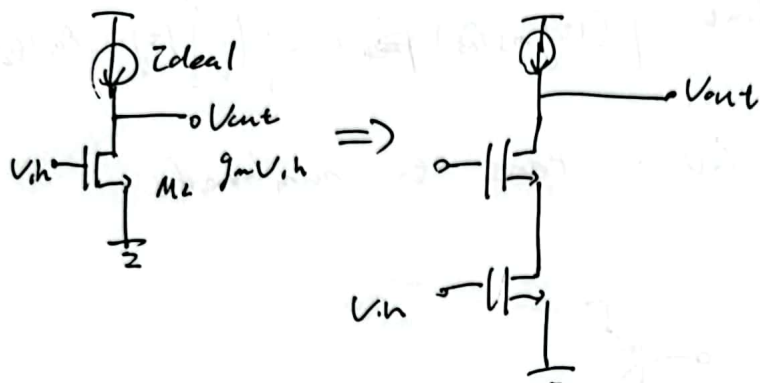


Cas Code Amp.


Use the method we derive just now



Quiz:

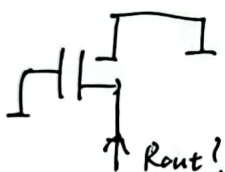


2个电阻 = 1个电阻
结论得出

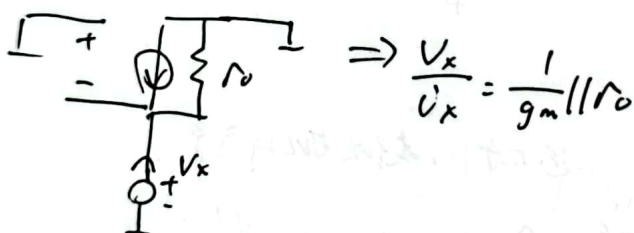

$$A_{m2} = g_{m2}$$

(b)


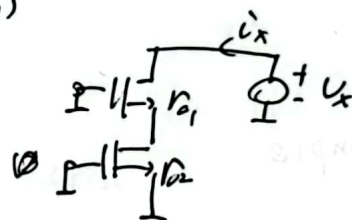


$$R_{out} = \frac{V_x}{I_x} = (1 + g_{m1} r_{o1}) r_{o2} + r_{o1}$$


$$\Rightarrow A_v = -g_{m2} [(1 + g_{m1} r_{o1}) r_{o2} + r_{o1}]$$

$$= -g_{m1} r_{o1} \cdot g_{m2} r_{o2}$$

Example

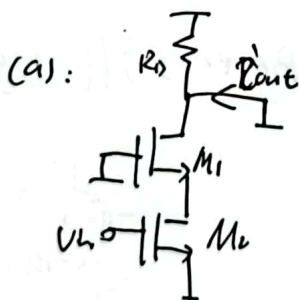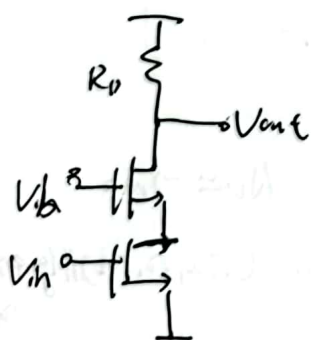
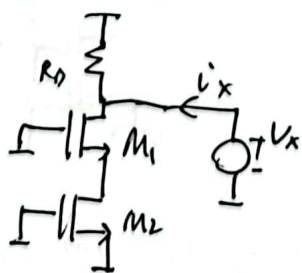
$$\frac{I_{out}}{V_{in}} = \frac{g_{m2} V_{in}}{V_{in}} = g_{m2}$$




$$\frac{V_x}{V_{in}} = [(1 + g_{m1} r_{o1}) r_{o2} + r_{o1}] || R_D$$

$$\therefore A_v = -g_{m2} [R_D || ((1 + g_{m1} r_{o1}) r_{o2} + r_{o1})]$$

$$R_D \Rightarrow r_{o3}$$

Cascode Amp with Cascode Load

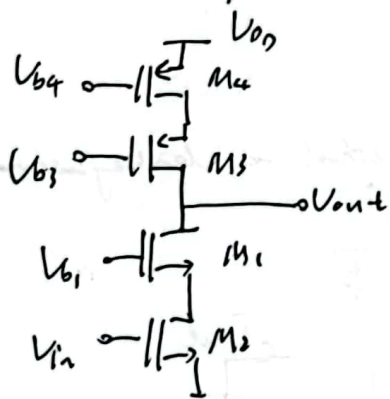


$$(a) A_m = g_{m2}$$


$$(b) R_{out} = \left\{ (1 + g_{m3} r_{o3}) g_{m4} r_{o4} \right\} \parallel \left\{ (1 + g_{m1} r_{o1}) g_{m2} r_{o2} \right\}$$

A_v : tens to hundreds

Bipolar Cascode Amp

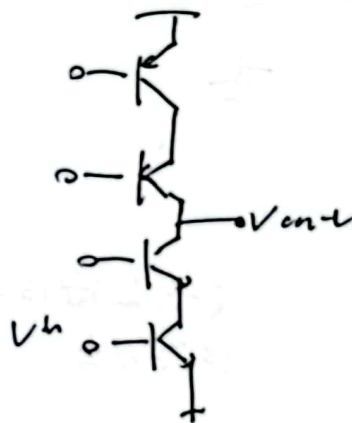


Example

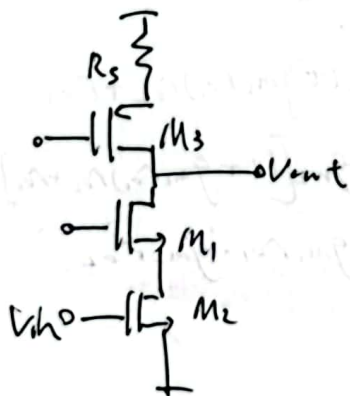


这不行，类似可以写为：

$$R_{out} = \left((1 + g_{m3} r_{o3}) R_s + r_{o3} \right) \parallel \left((1 + g_{m1} r_{o1}) r_{o2} + r_{o1} \right)$$

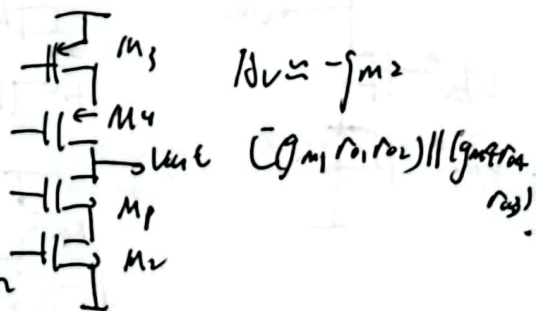
$$\approx (g_{m3} r_{o3} R_s + r_{o3}) \parallel (g_{m1} r_{o1} r_{o2})$$




Cascode Amp with P-Type Input

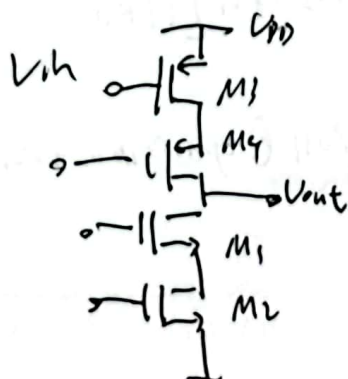

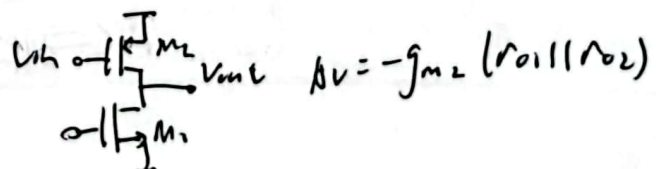
$$A_v = -g_{m3} \left[(g_{m1} r_{o1} r_{o2}) \parallel (g_{m4} r_{o4} r_{o3}) \right]$$



• Problem of Biasing Current Sources

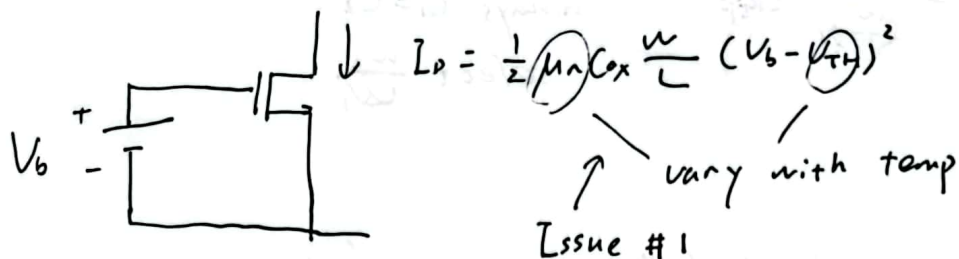

How to generate V_b :


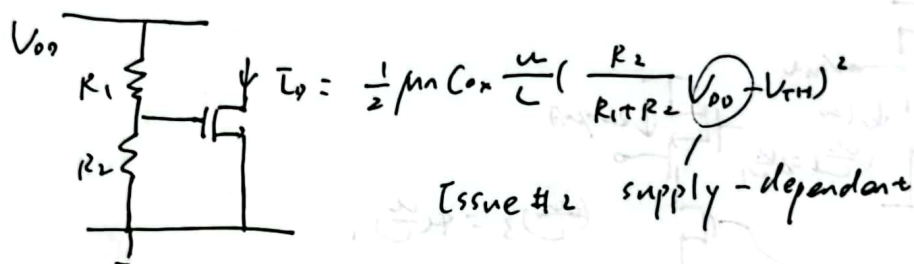


That's why we need a current ~~source~~ mirror.

• Current Mirror

First, build one "golden" current source, using a "Bandgap" circuit.

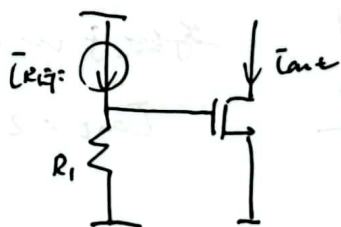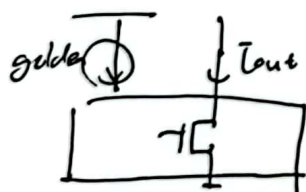Next, we "copy" this current source to build many others.





$$I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{REF} - V_{TH})^2$$

↑ vary with temp

So, how to copy a I_{REF} ?

Observations.

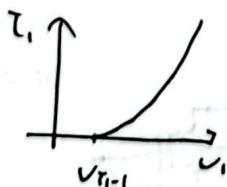
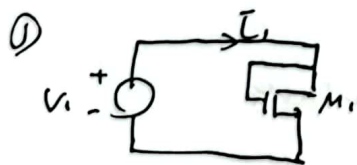


If M_1 is on, it is in sat.


$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_i - V_{TH})^2$$


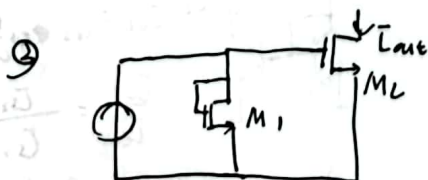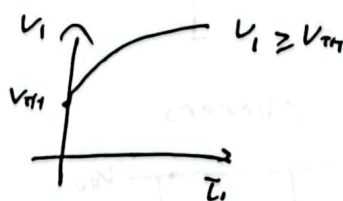
$$V_i = \sqrt{\frac{2 I_1}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$


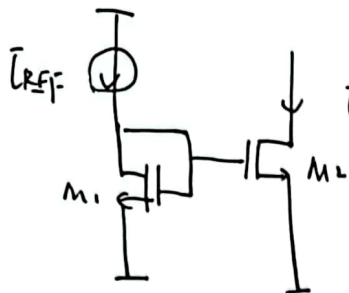
$$I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_i - V_{TH})^2 = \left(\frac{W}{L} \right)_2 \bar{I}_1 \quad \text{Current Mirror}$$




$$I_{out} = \frac{(\frac{W}{L})_2}{(\frac{W}{L})_1} I_{REF}$$

always $L_1 = L_2$

select $\frac{W_2}{W_1}$

Also, Example

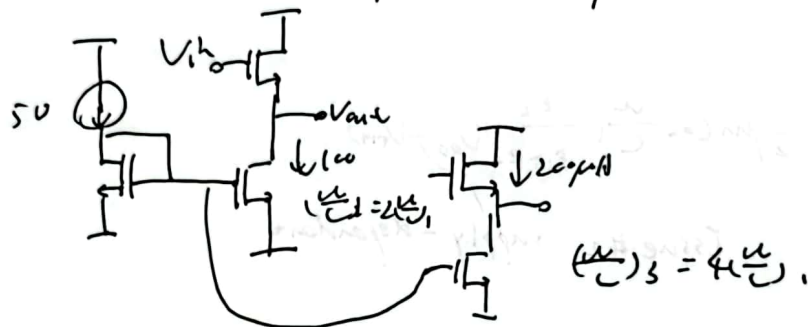A circuit include two source followers biased at $100\mu A$ and $200\mu A$. We have a reference current of $50\mu A$.




Alternative perspective



$$\left. \begin{aligned} I_{D1} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH})^2 \\ I_{D2} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS} - V_{TH})^2 \end{aligned} \right\} \Rightarrow I_{D1} = I_{D2} \times \frac{(W/L)_1}{(W/L)_2}$$


Example

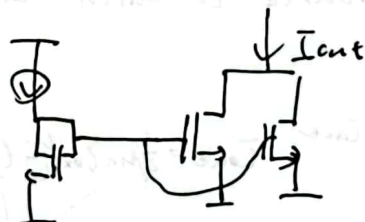

等效于 n double.


$$I_{out} = 2 I_{REF}$$

类似地, 设置参考电流

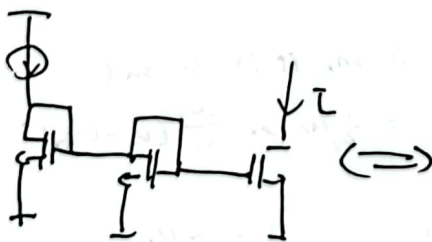


$$W = W_1 + W_2$$

PMOS Current Mirrors.

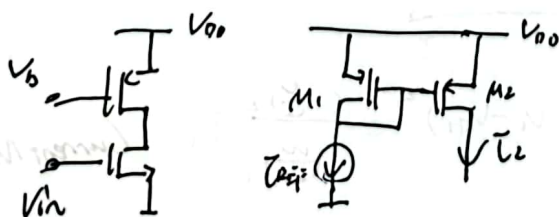

$$I_2 = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$

Bipolar Current Mirrors

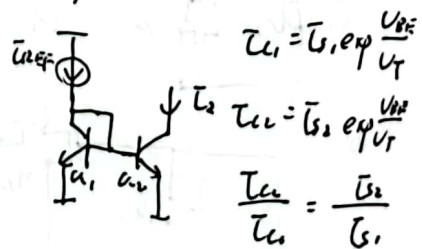

$$I_{C1} = I_S \exp \frac{V_{BE}}{V_T}$$


$$I_{C2} = I_S \exp \frac{V_{BE}}{V_T}$$

$$\frac{I_{C2}}{I_{C1}} = \frac{I_{S2}}{I_{S1}}$$

位置, I_{C1} 会小, 因为基极有电流.

Problem of Noise Coupling

from ECG

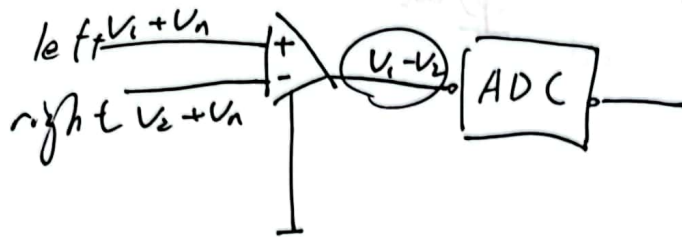


心电图通常有 50Hz/60Hz noise. 通过差分消除.

$V_1 - V_2$ has no 50Hz/60Hz noise.


Differential Signals.

(a) they vary by equal and opposite amounts

(b) they have the same average value

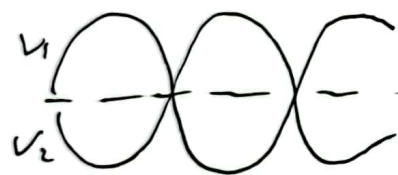

we call this the common mode.


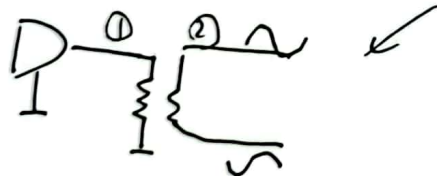


Generate the differential signals.

If the noise is added to the transmission line ^②, the differential ~~ps~~ can decrease it.

but if is added to the ①, no way.

The Differential pair

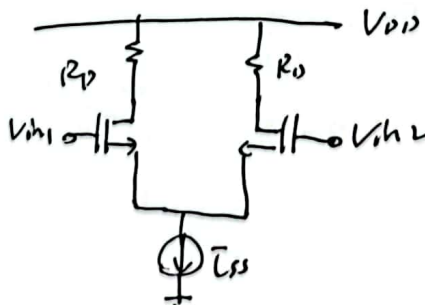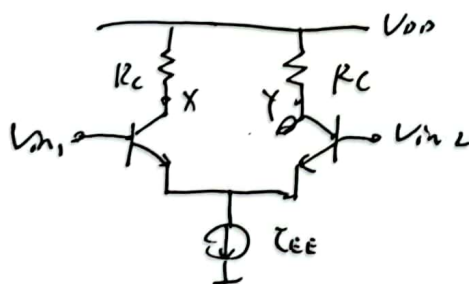


Bipolar Differential Pair.

Case I: $V_{in1} = V_{in2} = V_{cm}$

$$\bar{I}_{C1} = \bar{I}_{C2} = \frac{\bar{I}_{EE}}{2}$$
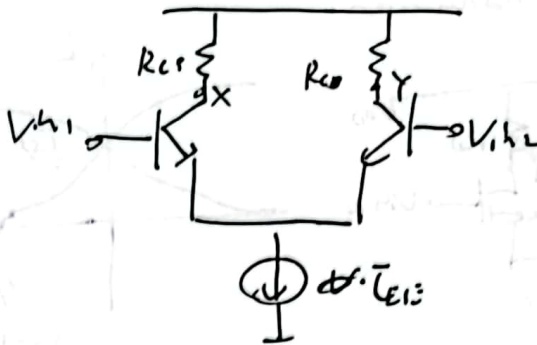
$$V_x = V_{cc} - \frac{\bar{I}_{EE}}{2} R_c = V_y$$



The differential pair rejects perturbations in the input CM level

Case II:

$$V_{in1} > V_{in2}$$


考虑极端的状况.

$$V_{in1} - V_{BE} > V_{in2} \Rightarrow Q_2 \text{ is off.}$$

$$\therefore \bar{I}_{C1} = \bar{I}_{EE}, \bar{I}_{C2} = 0$$


$$V_x = V_{cc} - R_c \bar{I}_{EE} \quad V_y = V_{cc}$$

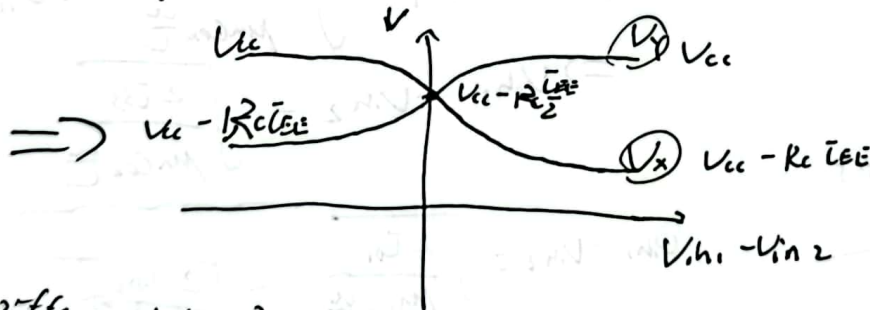Case III: $V_{in1} < V_{in2}$ 同理: $\bar{I}_{C1} = 0, \bar{I}_{C2} = \bar{I}_{EE}, V_x = V_{cc}, V_y = V_{cc} - R_c \bar{I}_{EE}$



MOS Differential Pair.

General Properties.

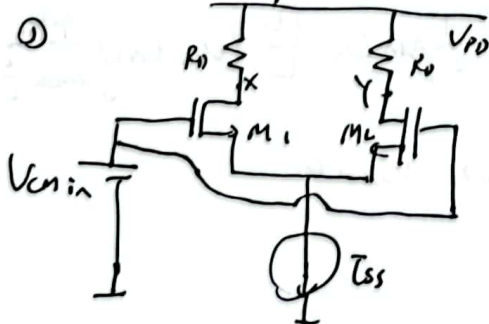

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_x = V_y = V_{DD} - R_D \frac{I_{SS}}{2}$$

$$V_{GS1} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

If $V_{in1} = V_{in2}$, the diff pair is in equilibrium. The equilibrium overdrive voltage:

$$V_{GS1} - V_{TH} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

V_{in} change, nothing change

